

40.3.2. A7


# Transistor Circuit Approximations

Third Edition

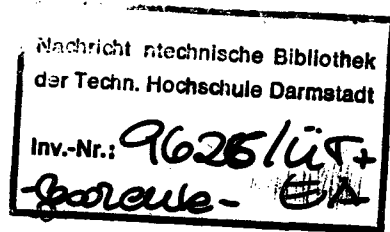**Albert Paul Malvino, Ph.D.**

Foothill College  
Los Altos Hills, California

West Valley College  
Saratoga, California



**Gregg Division  
McGraw-Hill Book Company**

New York	Atlanta	Dallas
St. Louis	San Francisco	Auckland
Bogotá	Düsseldorf	Johannesburg
London	Madrid	Mexico
Montreal	New Delhi	Panama
Paris	São Paulo	Singapore
Sydney	Tokyo	Toronto

# Contents

**Preface** xi

**Chapter 1 Semiconductor Physics 1**

1-1. Germanium and silicon atoms 1-2. Crystals  
1-3. Conduction in pure silicon 1-4. Holes  
1-5. Extrinsic semiconductors 1-6. Semiconductor devices

**Chapter 2 Rectifier Diodes 12**

2-1. The *pn* junction 2-2. Forward and reverse bias  
2-3. The diode curve 2-4. The ideal diode 2-5. The second approximation  
2-6. The third approximation 2-7. Using the approximations  
2-8. Approximating reverse current

**Chapter 3 Special Diodes 30**

3-1. Light-emitting diodes 3-2. Photodiodes, isolators, and solar cells  
3-3. Schottky diodes  
3-4. Varactors 3-5. Zener diodes 3-6. Laser diodes  
3-7. Step-recovery diodes 3-8. Backward diodes  
3-9. Tunnel diodes

## Contents

### **Chapter 4 Diode Applications 47**

4-1. The half-wave rectifier 4-2. The center-tap rectifier 4-3. The bridge rectifier 4-4. The capacitor-input filter 4-5. L and  $\pi$  filters 4-6. Voltage multipliers 4-7. The zener regulator 4-8. Clippers and clampers 4-9. Logic gates

### **Chapter 5 Small-Signal Diode Approximations 74**

5-1. The superposition theorem 5-2. The ac resistance of a diode 5-3. Applying superposition to diode circuits

### **Chapter 6 Common-Base Approximations 85**

6-1. Structure 6-2. Biasing the bipolar transistor 6-3. Common-base collector curves 6-4. Alpha and beta 6-5. The ideal transistor 6-6. Analyzing common-base amplifiers

### **Chapter 7 Common-Emitter Approximations 102**

7-1. The CE connection 7-2. Base bias 7-3. Voltage-divider bias 7-4. Exact formula for voltage-divider bias 7-5. Other biasing circuits 7-6. *pnp* Biasing 7-7. Upside-down biasing of *pnp* transistors 7-8. Analyzing common-emitter amplifiers 7-9. Swamping the emitter diode

### **Chapter 8 Common-Collector Approximations 137**

8-1. Voltage gain 8-2. Input impedance 8-3. Power gain 8-4. Source impedance 8-5. Using an emitter follower 8-6. The Darlington pair 8-7. The zener regulator

### **Chapter 9 Class A Power Amplifiers 152**

9-1. The ac load line of a CE amplifier 9-2. The ac load line of an emitter follower 9-3. The optimum  $Q$

point 9.4. Power formulas 9.5. Large-signal gain and impedance 9.6. Transistor power ratings

## **Chapter 10 Other Power Amplifiers 178**

10-1. Classes of operation 10-2. The current mirror 10-3. Biasing a class B push-pull amplifier 10-4. Class B push-pull emitter follower 10-5. A complete amplifier 10-6. The tuned class C amplifier 10-7. Switching operation

## **Chapter 11 Cascading Stages, Frequency Response, and $h$ Parameters 200**

11-1. RC coupling 11-2. Two-stage feedback 11-3. Inductive coupling 11-4. Transformer coupling 11-5. Direct coupling 11-6. The differential amplifier 11-7. Response of an RC-coupled amplifier 11-8. Lower CE cutoff frequencies 11-9. Transistor cutoff frequencies 11-10. Second-approximation formulas 11-11 Hybrid parameters 11-12. Approximate hybrid formulas 11-13. Exact hybrid formulas

## **Chapter 12 JFETs 232**

12-1. Construction and operation 12-2. Drain curves 12-3. JFET parameters 12-4. Self-bias 12-5. Current-source bias 12-6. JFET amplifiers 12-7. The JFET used as a switch

## **Chapter 13 MOSFETs 261**

13-1. Depletion-type MOSFET 13-2. Enhancement-type MOSFET 13-3. Biasing MOSFETs 13-4. The MOSFET as a driver and a load 13-5. MOS logic circuits 13-6. VMOS

## **Contents**

### **Chapter 14 Operational Amplifiers 281**

14-1. Generations of op amps 14-2. A simplified op-amp circuit 14-3. Op-amp specifications 14-4. Slew rate and power bandwidth 14-5. Negative feedback 14-6. The op amp as a noninverting amplifier 14-7. The op amp as an inverting amplifier 14-8. Op-amp applications

### **Chapter 15 Thyristors 314**

15-1. The ideal latch 15-2. The four-layer diode 15-3. The silicon-controlled rectifier 15-4. Variations of the SCR 15-5. Bidirectional thyristors 15-6. The unijunction transistor 15-7. UJT circuits

### **Chapter 16 Pulse and Digital Circuits 336**

16-1. The rectangular pulse 16-2. Effect of stray capacitance 16-3. Waveshaping circuits 16-4. Logic circuits 16-5. Digital integrated circuits 16-6. Multivibrators

### **Answers to Odd-Numbered Problems 357**

### **Appendix 361**

### **References for Further Reading 363**

### **Index 365**