

# Analog Circuit Design

A Tutorial Guide to Applications and Solutions

Edited by

Bob Dobkin

Jim Williams



Amsterdam • Boston • Heidelberg • London • New York • Oxford  
Paris • San Diego • San Francisco • Singapore • Sydney • Tokyo  
Newnes is an imprint of Elsevier



Publisher's Note . . . . .	xi
Acknowledgments . . . . .	xiii
Introduction . . . . .	xiv
Foreword . . . . .	xvi

## **PART 1** Power Management

<b>Section 1</b> Power Management Tutorials . . . . .	<b>3</b>
<b>1</b> Ceramic input capacitors can cause overvoltage transients . . . . .	<b>4</b>
<b>2</b> Minimizing switching regulator residue in linear regulator outputs . . . . .	<b>7</b>
<b>3</b> Power conditioning for notebook and palmtop systems . . . . .	<b>18</b>
<b>4</b> 2-Wire virtual remote sensing for voltage regulators . . . . .	<b>35</b>
<b>Section 2</b> Switching Regulator Design . . . . .	<b>57</b>
<b>5</b> LT1070 design manual . . . . .	<b>59</b>
<b>6</b> Switching regulators for poets . . . . .	<b>124</b>
<b>7</b> Step-down switching regulators . . . . .	<b>142</b>
<b>8</b> A monolithic switching regulator with 100 $\mu$ V output noise . . . . .	<b>169</b>
<b>9</b> Powering complex FPGA-based systems using highly integrated DC/DC $\mu$ Module regulator systems . . . . .	<b>225</b>
<b>10</b> Powering complex FPGA-based systems using highly integrated DC/DC $\mu$ Module regulator systems . . . . .	<b>229</b>
<b>11</b> Diode turn-on time induced failures in switching regulators . . . . .	<b>232</b>
<b>Section 3</b> Linear Regulator Design . . . . .	<b>249</b>
<b>12</b> Performance verification of low noise, low dropout regulators . . . . .	<b>250</b>
<b>Section 4</b> High Voltage and High Current Applications . . . . .	<b>267</b>
<b>13</b> Parasitic capacitance effects in step-up transformer design . . . . .	<b>268</b>
<b>14</b> High efficiency, high density, PolyPhase converters for high current applications . . . . .	<b>272</b>
<b>Section 5</b> Powering Lasers and Illumination Devices . . . . .	<b>287</b>
<b>15</b> Ultracompact LCD backlight inverters . . . . .	<b>288</b>
<b>16</b> A thermoelectric cooler temperature controller for fiber optic lasers . . . . .	<b>308</b>
<b>17</b> Current sources for fiber optic lasers . . . . .	<b>319</b>
<b>18</b> Bias voltage and current sense circuits for avalanche photodiodes . . . . .	<b>338</b>

Section 6 Automotive and Industrial Power Design . . . . .	367
19 Developments in battery stack voltage measurement . . . . .	368
 <b>Part 2 Data Conversion, Signal Conditioning and High Frequency/RF</b>	
Section 1 Data Conversion . . . . .	393
20 Some techniques for direct digitization of transducer outputs . . . . .	394
21 The care and feeding of high performance ADCs: get all the bits you paid for . . . . .	406
22 A standards lab grade 20-bit DAC with 0.1ppm/°C drift . . . . .	414
23 Delta sigma ADC bridge measurement techniques . . . . .	461
24 1ppm settling time measurement for a monolithic 18-bit DAC . . . . .	480
Section 2 Signal Conditioning . . . . .	515
25 Applications for a switched-capacitor instrumentation building block . . . . .	518
26 Application considerations and circuits for a new chopper-stabilized op amp . . . . .	532
27 Designing linear circuits for 5V single supply operation . . . . .	550
28 Application considerations for an instrumentation lowpass filter. . . . .	563
29 Micropower circuits for signal conditioning . . . . .	574
30 Thermocouple measurement. . . . .	596
31 Take the mystery out of the switched-capacitor filter . . . . .	614
32 Bridge circuits . . . . .	638
33 High speed amplifier techniques . . . . .	679
34 A seven-nanosecond comparator for single supply operation . . . . .	804
35 Understanding and applying voltage references . . . . .	839
36 Instrumentation applications for a monolithic oscillator . . . . .	850
37 Slew rate verification for wideband amplifiers . . . . .	868
38 Instrumentation circuitry using RMS-to-DC converters . . . . .	879
39 775 nanovolt noise measurement for a low noise voltage reference . . . . .	896
Section 3 High Frequency/RF Design . . . . .	905
40 LT5528 WCDMA ACPR, AltCPR and noise measurements . . . . .	906
41 Measuring phase and delay errors accurately in I/Q modulators . . . . .	910
Index . . . . .	917