

HIGH-POWER CONVERTERS AND AC DRIVES

BinWu

•IEEE

IEEE PRESS

 **WILEY-
INTERSCIENCE**

A John Wiley & Sons, Inc., Publication

Contents

Preface	xiii
Part One Introduction	1
1. Introduction	3
1.1 Introduction	3
1.2 Technical Requirements and Challenges	5
1.2.1 Line-Side Requirements	5
1.2.2 Motor-Side Challenges	6
1.2.3 Switching Device Constraints	7
1.2.4 Drive System Requirements	8
1.3 Converter Configurations	8
1.4 MV Industrial Drives	10
1.5 Summary	13
References	13
Appendix	14
2. High-Power Semiconductor Devices	17
2.1 Introduction	17
2.2 High-Power Switching Devices	18
2.2.1 Diodes	18
2.2.2 Silicon-Controlled Rectifier (SCR)	18
2.2.3 Gate Turn-Off (GTO)Thyristor	21
2.2.4 Gate-Commutated Thyristor (GCT)	23
2.2.5 Insulated Gate Bipolar Transistor (IGBT)	26
2.2.6 Other Switching Devices	28
2.3 Operation of Series-Connected Devices	28
2.3.1 Main Causes of Voltage Unbalance	29
2.3.2 Voltage Equalization for GCTs	29
2.3.3 Voltage Equalization for IGBTs	31
2.4 Summary	32
References	33

Part Two	Multipulse Diode and SCR Rectifiers	35
3.	Multipulse Diode Rectifiers	37
3.1	Introduction	37
3.2	Six-Pulse Diode Rectifier	38
3.2.1	Introduction	38
3.2.2	Capacitive Load	40
3.2.3	Definition of THD and PF	43
3.2.4	Per-Unit System	45
3.2.5	THD and PF of Six-Pulse Diode Rectifier	45
3.3	Series-Type Multipulse Diode Rectifiers	47
3.3.1	12-Pulse Series-Type Diode Rectifier	47
3.3.2	18-Pulse Series-Type Diode Rectifier	51
3.3.3	24-Pulse Series-Type Diode Rectifier	54
3.4	Separate-Type Multipulse Diode Rectifiers	57
3.4.1	12-Pulse Separate-Type Diode Rectifier	57
3.4.2	18- and 24-Pulse Separate-Type Diode Rectifiers	61
3.5	Summary	61
	References	61
4.	Multipulse SCR Rectifiers	65
4.1	Introduction	65
4.2	Six-Pulse SCR Rectifier	65
4.2.1	Idealized Six-Pulse Rectifier	66
4.2.2'	Effect of Line Inductance	70
4.2.3	Power Factor and THD	72
4.3	12-Pulse SCR Rectifier	74
4.3.1	Idealized 12-Pulse Rectifier	75
4.3.2	Effect of Line and Leakage Inductances	78
4.3.3	THD and PF	79
4.4	18- and 24-Pulse SCR Rectifiers	79
4.5	Summary	81
	References	81
5.	Phase-Shifting Transformers	83
5.1	Introduction	83
5.2	Y/Z Phase-Shifting Transformers	83
5.2.1	Y/Z-1 Transformers	83
5.2.2	Y/Z-2 Transformers	85
5.3	A/Z Transformers	87
5.4	Harmonic Current Cancellation	88
5.4.1	Phase Displacement of Harmonic Currents	88
5.4.2	Harmonic Cancellation	90
5.5	Summary	92

Part Two	Multipulse Diode and SCR Rectifiers	35
3.	Multipulse Diode Rectifiers	37
3.1	Introduction	37
3.2	Six-Pulse Diode Rectifier	38
3.2.1	Introduction	38
3.2.2	Capacitive Load	40
3.2.3	Definition of THD and PF	43
3.2.4	Per-Unit System	45
3.2.5	THD and PF of Six-Pulse Diode Rectifier	45
3.3	Series-Type Multipulse Diode Rectifiers	47
3.3.1	12-Pulse Series-Type Diode Rectifier	47
3.3.2	18-Pulse Series-Type Diode Rectifier	51
3.3.3	24-Pulse Series-Type Diode Rectifier	54
3.4	Separate-Type Multipulse Diode Rectifiers	57
3.4.1	12-Pulse Separate-Type Diode Rectifier	57
3.4.2	18- and 24-Pulse Separate-Type Diode Rectifiers	61
3.5	Summary	61
	References	61
4.	Multipulse SCR Rectifiers	65
4.1	Introduction	65
4.2	Six-Pulse SCR Rectifier	65
4.2.1	Idealized Six-Pulse Rectifier	66
4.2.2	Effect of Line Inductance	70
4.2.3	Power Factor and THD	72
4.3	12-Pulse SCR Rectifier	74
4.3.1	Idealized 12-Pulse Rectifier	75
4.3.2	Effect of Line and Leakage Inductances	78
4.3.3	THD and PF	79
4.4	18- and 24-Pulse SCR Rectifiers	79
4.5	Summary	81
	References	81
5.	Phase-Shifting Transformers	83
5.1	Introduction	83
5.2	Y/Z Phase-Shifting Transformers	83
5.2.1	Y/Z-1 Transformers	83
5.2.2	Y/Z-2 Transformers	85
5.3	A/Z Transformers	87
5.4	Harmonic Current Cancellation	88
5.4.1	Phase Displacement of Harmonic Currents	88
5.4.2	Harmonic Cancellation	90
5.5	Summary	92

Part Three	Multilevel Voltage Source Converters	93
6.	Two-Level Voltage Source Inverter	95
6.1	Introduction	95
6.2	Sinusoidal PWM	95
6.2.1	Modulation Scheme	95
6.2.2	Harmonic Content	96
6.2.3	Overmodulation	99
6.2.4	Third Harmonic Injection PWM	99
6.3	Space Vector Modulation	101
6.3.1	Switching States	101
6.3.2	Space Vectors	101
6.3.3	Dwell Time Calculation	104
6.3.4	Modulation Index	106
6.3.5	Switching Sequence	107
6.3.6	Spectrum Analysis	108
6.3.7	Even-Order Harmonic Elimination	111
6.3.8	Discontinuous Space Vector Modulation	115
6.4	Summary	116
	References	117
7.	Cascaded H-Bridge Multilevel Inverters	119
7.1	Introduction	119
7.2	H-Bridge Inverter	119
7.2.1	Bipolar Pulse-Width Modulation	120
7.2.2	Unipolar Pulse-Width Modulation	121
7.3	Multilevel Inverter Topologies	123
7.3.1	CHB Inverter with Equal dc Voltage	123
7.3.2	H-Bridges with Unequal dc Voltages	126
7.4	Carrier Based PWM Schemes	127
7.4.1	Phase-Shifted Multicarrier Modulation	127
7.4.2	Level-Shifted Multicarrier Modulation	131
7.4.3	Comparison Between Phase- and Level-Shifted PWM Schemes	136
7.5	Staircase Modulation	139
7.6	Summary	141
	References	142
8.	Diode-Clamped Multilevel Inverters	143
8.1	Introduction	143
8.2	Three-Level Inverter	143
8.2.1	Converter Configuration	143
8.2.2	Switching State	144

8.2.3	Commutation	145
8.3	Space Vector Modulation	148
8.3.1	Stationary Space Vectors	149
8.3.2	Dwell Time Calculation	149
8.3.3	Relationship Between V_{ref} Location and Dwell Times	154
8.3.4	Switching Sequence Design	154
8.3.5	Inverter Output Waveforms and Harmonic Content	160
8.3.6	Even-Order Harmonic Elimination	160
8.4	Neutral-Point Voltage Control	164
8.4.1	Causes of Neutral-Point Voltage Deviation	165
8.4.2	Effect of Motoring and Regenerative Operation	165
8.4.3	Feedback Control of Neutral-Point Voltage	166
8.5	Other Space Vector Modulation Algorithms	167
8.5.1	Discontinuous Space Vector Modulation	167
8.5.2	SVM Based on Two-Level Algorithm	168
8.6	High-Level Diode-Clamped Inverters	168
8.6.1	Four- and Five-Level Diode-Clamped Inverters	169
8.6.2	Carrier-Based PWM	170
8.7	Summary	173
	References	175
	Appendix	176

9. Other Multilevel Voltage Source Inverters 179

9.1	Introduction	179
9.2	NPC/H-Bridge Inverter	179
9.2.1	Inverter Topology	179
9.2.2	Modulation Scheme	180
9.2.3	Waveforms and Harmonic Content	181
9.3	Multilevel Flying-Capacitor Inverters	183
9.3.1	Inverter Configuration	183
9.3.2	Modulation Schemes	184
9.4	Summary	186
	References	186

Part Four PWM Current Source Converters 187

10. PWM Current Source Inverters 189

10.1	Introduction	189
10.2	PWM Current Source Inverter	190
/	10.2.1 Trapezoidal Modulation	191
	10.2.2 Selective Harmonic Elimination	194

10.3	Space Vector Modulation	200
10.3.1	Switching States	200
10.3.2	Space Vectors	201
10.3.3	Dwell Time Calculation	203
10.3.4	Switching Sequence	205
10.3.5	Harmonic Content	208
10.3.6	SVM Versus TPWM and SHE	209
10.4	Parallel Current Source Inverters	209
10.4.1	Inverter Topology	209
10.4.2	Space Vector Modulation for Parallel Inverters	210
10.4.3	Effect of Medium Vectors on dc Currents	212
10.4.4	dc Current Balance Control	213
10.4.5	Experimental Verification	214
10.5	Load-Commutated Inverter (LCI)	215
10.6	Summary	216
	References	217
	Appendix	218

11. PWM Current Source Rectifiers

219

11.1	Introduction	219
11.2	Single-Bridge Current Source Rectifier	219
11.2.1	Introduction	219
11.2.2	Selective Harmonic Elimination	220
11.2.3	Rectifier dc Output Voltage	225
11.2.4	Space Vector Modulation	227
11.3	Dual-Bridge Current Source Rectifier	227
11.3.1	Introduction	227
11.3.2	PWM Schemes	228
11.3.3	Harmonic Contents	229
11.4	Power Factor Control	231
11.4.1	Introduction	231
11.4.2	Simultaneous a and m_a Control	232
11.4.3	Power Factor Profile	235
11.5	Active Damping Control	236
11.5.1	Introduction	236
11.5.2	Series and Parallel Resonant Modes	237
11.5.3	Principle of Active Damping	238
11.5.4	LC Resonance Suppression	240
11.5.5	Harmonic Reduction	242
11.5.6	Selection of Active Damping Resistance	245
11.6	Summary	246
	References	247
	Appendix	248

Part Five	High-Power AC Drives	251
12.	Voltage Source Inverter-Fed Drives	253
12.1	Introduction	253
12.2	Two-Level VBSI-Based MV Drives	253
12.2.1	Power Converter Building Block	253
12.2.2	Two-Level VSI with Passive Front End	254
12.3	Neutral-Point Clamped (NPC) Inverter-Fed Drives	257
12.3.1	GCT-Based NPC Inverter Drives	257
12.3.2	IGBT-Based NPC Inverter Drives	260
12.4	Multilevel Cascaded H-Bridge (CHB) Inverter-Fed Drives	261
12.4.1	CHB Inverter-Fed Drives for 2300-V/4160-V Motors	261
12.4.2	CHB Inverter Drives for 6.6-kV/1.8-kV Motors	264
12.5	NPC/H-Bridge Inverter-Fed Drives	264
12.6	Summary	265
	References	265
13.	Current Source Inverter-Fed Drives	269
13.1	Introduction	269
13.2	CSI Drives with PWM Rectifiers	269
13.2.1	CSI Drives with Single-bridge PWM Rectifier	269
13.2.2	CSI Drives for Custom Motors	273
13.2.3	CSI Drives with Dual-Bridge PWM Rectifier	275
13.3	Transformerless CSI Drive for Standard AC Motors	276
13.3.1	CSI Drive Configuration	276
13.3.2	Integrated dc Choke for Common-Mode Voltage Suppression	277
13.4	CSI Drive with Multipulse SCR Rectifier	279
13.4.1	CSI Drive with 18-Pulse SCR Rectifier	279
13.4.2	Low-Cost CSI Drive with 6-Pulse SCR Rectifier	280
13.5	LCI Drives for Synchronous Motors	281
13.5.1	LCI Drives with 12-Pulse Input and 6-Pulse Output	281
13.5.2	LCI Drives with 12-Pulse Input and 12-Pulse Output	282
13.6	Summary	282
	References	283
14.	Advanced Drive Control Schemes	285
14.1	Introduction	285
14.2	Reference Frame Transformation	285
14.2.1	$abcl dq$ Frame Transformation	286
/ 14.2.2	$3/2$ Stationary Transformation	288
14.3	Induction Motor Dynamic Models	288
14.3.1	Space Vector Motor Model	288

14.3.2	<i>dq</i> -Axis Motor Model	290
14.3.3	Induction Motor Transient Characteristics	291
14.4	Principle of Field-Oriented Control (FOC)	296
14.4.1	Field Orientation	296
14.4.2	General Block Diagram of FOC	297
14.5	Direct Field-Oriented Control	298
14.5.1	System Block Diagram	298
14.5.2	Rotor Flux Calculator	299
14.5.3	Direct FOC with Current-Controlled VSI	301
14.6	Indirect Field-Oriented Control	305
14.7	FOC for CSI-Fed Drives	307
14.8	Direct Torque Control	309
14.8.1	Principle of Direct Torque Control	310
14.8.2	Switching Logic	311
14.8.3	Stator Flux and Torque Calculation	313
14.8.4	DTC Drive Simulation	314
14.8.5	Comparison Between DTC and FOC Schemes	316
14.9	Summary	316
	References	317

Abbreviations **319**

Appendix Projects for Graduate-Level Courses **321**

P. 1	Introduction	321
P. 2	Sample Project	322
P. 3	Answers to Sample Project	324

Index **329**

About the Author **333**