


Designing with TTL Integrated Circuits

Prepared by the IC Applications Staff of
Texas Instruments Incorporated

Edited by
Robert L. Morris and John R. Miller

Contributors

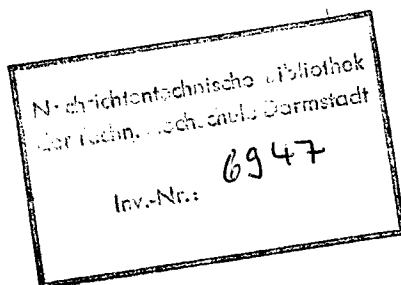W. D. Anderson
A. G. Douce
R. C. Grimes
W. R. Heniford
R. L. Morris
R. F. Schweitzer
S. Wolff



McGRAW-HILL BOOK COMPANY

New York St. Louis San Francisco Auckland Düsseldorf
Johannesburg Kuala Lumpur London Mexico Montreal
New Delhi Panama Paris São Paulo Singapore
Sydney Tokyo Toronto

Contents

<i>Preface</i>	v
Chapter 1. Introduction to Digital Logic	1
1.1 The Binary System	1
1.2 Logic Circuits	2
1.3 Use of Logic Gates	4
1.4 Logic Designation	8
1.5 Comparison of Logic Types	8
1.6 Levels of Integrated-circuit Complexity	13
Chapter 2. Series 54/74 Overview	15
2.1 Typical Characteristics	15
2.2 Standard Series 54/74 TTL	16
2.3 Series 54/74 Low-power TTL	18
2.4 Series 54H/74H High-speed TTL	18
2.5 Series 54S/74S Schottky-clamped TTL	21
Chapter 3. Circuit Analysis and Characteristics of Series 54/74	23
3.1 Basic TTL Operation	23
3.2 TTL Advantages	24
3.3 Circuit Parameters	25
3.4 Circuit Characteristics of Specialized Gates	45
APPENDIX TO CHAPTER 3: <i>TTL Loading Rules</i>	57
Chapter 4. Extended-range Operation	67
4.1 Integrated-circuit Components	67
4.2 Device Reaction to External Influences	69
4.3 Voltage Breakdown for Input and Output	79

Chapter 5. Noise Considerations	83
5.1 Noise Types and Control Methods	84
5.2 Shielding	84
5.3 Grounding and Decoupling	85
5.4 Cross Talk	93
5.5 Transmission-line Reflections	96
Chapter 6. Combinational Logic Design	107
6.1 Basic Functions	107
6.2 Postulates and Theorems	108
6.3 Logic Expressions	109
6.4 Simplification and Minimization	110
6.5 Practical Logic Gates	114
6.6 Analysis of Logic Circuits	115
6.7 Implementation of Logic Expressions	118
6.8 Implementation of Fundamental Logic Functions	119
6.9 Combinational Logic Applications	131
Bibliography	159
Chapter 7. Flip-flops	161
7.1 Flip-flop Types	163
7.2 Series 54/74 Flip-flops	171
7.3 Flip-flop Applications	173
Chapter 8. Decoders	181
8.1 Decoder Theory	181
8.2 Series 54/74 Decoders and Decoder/Drivers	189
8.3 Applications of Decoders	202
Chapter 9. Arithmetic Elements	211
9.1 Addition of Binary Numbers	211
9.2 Parallel Binary Addition	213
9.3 Serial Binary Adder	214
9.4 Series 54/74 TTL Arithmetic Elements	214
9.5 Binary Representations for Computer Arithmetic	220
9.6 Addition and Subtraction of Decimal Numbers with Binary Representations	224
9.7 Fast Binary Addition	235
9.8 Adder Applications to Binary Number Representation Conversion	240

	Contents	ix
Chapter 10. Counters		243
10.1 Ripple Counters		243
10.2 Synchronous Counters		248
10.3 Series 54/74 Counters		254
10.4 Counter Implementation and Applications		271
Chapter 11. Shift Registers		285
11.1 SN54/74 Shift Registers		286
11.2 Shift Register Counters and Generators		292
11.3 Other Shift Register Applications		305
Chapter 12. Other Applications		309
12.1 A Simple Binary Multiplier		309
12.2 12-hour Digital Clock		313
12.3 Serial Gray Code to Binary Conversion		313
12.4 Modulo-360 Adder		315
<i>Index</i>		319