

George J. Wakileh

Power Systems Harmonics

Fundamentals, Analysis
and Filter Design

With 263 Figures



Springer

Contents

1.	Introduction	1
2.	Fundamentals of Harmonics	5
2.1	Introduction	5
2.2	Examples of Harmonic Waveforms	5
2.3	Representation of Harmonics	7
2.4	Characteristics of Harmonics in Power Systems	10
2.4.1	Symmetry	10
2.4.2	Phase Sequence	13
2.4.3	Independence	15
2.5	Measures of Harmonic Distortion	15
2.5.1	RMS Voltage and Current	16
2.5.2	Voltage and Current Distortion Factors	16
2.5.3	Active (Real) and Reactive Power	19
2.5.4	Apparent Power	20
2.5.5	Distortion Power	20
2.5.6	Power Factor	20
2.5.7	Current and Voltage Crest Factors	21
2.5.8	Telephone Interference and the $I \cdot T$ Product	21
2.6	Power in Passive Elements	23
2.6.1	Power in a Pure Resistance	23
2.6.2	Power in a Pure Inductance	24
2.6.3	Power in a Pure Capacitance	25
2.7	Calculation of Distortion	25
2.8	Resonance	26
2.8.1	Series Resonance	27
2.8.2	Parallel Resonance	28
2.9	Capacitor Banks and Reactive Power Supply	30
2.10	Capacitor Banks and Power Factor Correction	35
2.11	Bus Voltage Rise and Resonance	37
2.12	Harmonics in Transformers	40
2.12.1	Delta-Connected Primaries	40
2.12.2	Wye-Connected Primaries	40
2.13	Summary	41

Problems	41
3. Harmonics in Power Systems – Their Causes	45
3.1 Introduction	45
3.2 Sources of Harmonics	45
3.3 Transformers	46
3.4 Rotating Machines	46
3.5 Fluorescent Lights	46
3.6 Static VAR Compensators	47
3.7 Cycloconverters	47
3.8 Single-Phase Controlled Rectifiers	48
3.8.1 Effect of ac Line Reactance	49
3.8.2 Zero dc Reactance ($L_d = 0$)	50
3.8.3 Zero dc Reactance ($L_d = 0$) – The Special Case $\alpha = 0$	54
3.8.4 Continuous Current Case (Large L_d)	56
3.8.5 Discontinuous Current Case (Small L_d)	64
3.9 Three-Phase Power Converters	66
3.9.1 DC / AC Inverters	66
3.9.2 Battery Converters	66
3.9.3 Six-Pulse Converters	66
3.9.4 Twelve-Pulse Converters	71
3.9.5 p-Pulse Converters	73
3.9.6 Typical Harmonic Spectra	74
3.9.6.1 Six-Pulse Converters	74
3.9.6.2 Twelve-Pulse Converters	75
3.9.6.3 Twenty-Four-Pulse Converters	75
3.10 Summary	78
Problems	78
4. Effects of Harmonic Distortion on Power Systems	81
4.1 Introduction	81
4.2 Thermal Losses in a Harmonic Environment	81
4.2.1 Copper Losses	81
4.2.2 Iron (Core) Losses	82
4.2.3 Dielectric (Insulation) Loss	83
4.3 Harmonic Effects on Power System Equipment	84
4.4 Capacitor Banks	85
4.4.1 Harmonic Amplification	85
4.5 Transformers	90
4.6 Rotating Machines	91
4.6.1 Induced EMF	92
4.6.2 Chorded (Fractional-Pitch) Windings	94
4.6.3 Distributed Windings	94
4.6.4 The Winding Factor	96
4.6.5 Induced EMF and Voltage Total Harmonic Distortion	96

4.7	Protection, Communication and Electronic Equipment	103
4.8	Summary	103
	Problems	103
5.	Mitigation of Power System Harmonics	105
5.1	Introduction	105
5.2	Harmonic Filters	105
5.2.1	Series-Tuned Filters	106
5.2.2	Double Band-Pass Filters	106
5.2.3	Damped Filters	106
5.2.4	Detuned (Anti-Resonant) Filters	106
5.2.5	Active Filters	107
5.3	Power Converters	107
5.4	Transformers	108
5.5	Rotating Machines	110
5.6	Capacitor Banks	111
5.7	Harmonic Filter Design	114
5.7.1	Series-Tuned Filters	116
5.7.2	Second-Order Damped Filters	121
5.7.3	Impedance Plots for Filter Banks	123
5.7.3.1	Impedance Plots for a Three-Branch 33 kV Filter	123
5.7.3.2	Impedance Plots for a Four-Branch 20 kV Filter	125
5.7.3.3	Impedance Plots for a Five-Branch 690 V Filter	128
5.8	Active Filters	130
5.9	Summary	135
	Problems	135
6.	Limits of Harmonic Distortion	137
6.1	Introduction	137
6.2	Voltage Harmonic Distortion Limits	137
6.2.1	IEEE Limits	137
6.2.2	IEC Limits	138
6.2.3	EN Limits	140
6.2.4	NORSOK Limits	141
6.3	Current Harmonic Distortion Limits	141
6.3.1	IEC Limits	141
6.3.2	IEEE Limits	143
6.3.3	NORSOK Limits	143

7.	Harmonic Studies – Modelling of System Components	145
7.1	Introduction	145
7.2	Impedance in the Presence of Harmonics	145
7.3	Skin Effect	146
7.4	Modelling of The High Voltage Grid	147
7.5	Generator Modelling	150
7.6	Modelling of Shunt Capacitor Banks	151
7.6.1	Shunt Capacitor Bank Model – Single-Phase Equivalent	153
7.7	Modelling of Series Capacitor Banks	153
7.8	Load Models	153
7.8.1	Series Load Model	154
7.8.2	Parallel Load Model	154
7.8.3	Load Model – Single-Phase Equivalent	155
7.8.4	Delta-Connected Loads	156
7.8.5	Wye-Connected Loads	157
7.8.6	General Load Model	158
7.9	Induction Motor Modelling	160
7.9.1	Induction Motor Model – Single-Phase Equivalent	164
7.10	Summary	165
	Problems	166
8.	Transformer Modelling	169
8.1	Introduction	169
8.2	Modelling of Two-Winding Transformers	169
8.2.1	Triplen Harmonics	170
8.2.2	Zero-Sequence Models	170
8.2.3	Y–Connected Windings	170
8.2.4	Δ –Connected Windings	171
8.2.5	ANSI Standard for Δ –Y / Y– Δ Transformers	172
8.2.6	Two-Winding Transformer Model – Single-Phase Equivalent	173
8.2.7	Phase and Sequence Admittance Matrices	175
8.2.7.1	Transformation and Turns Ratios	177
8.2.7.2	$Y_g - \Delta$ Transformers	178
8.2.7.3	Y– Δ Transformers	182
8.2.7.4	Δ – Y_g Transformers	184
8.2.7.5	Δ –Y Transformers	186
8.2.7.6	$\Delta - \Delta$ Transformers	188
8.2.7.7	$Y_g - Y_g$ Transformers	189
8.2.7.8	$Y_g - Y$ Transformers	191
8.2.7.9	Y– Y_g Transformers	192
8.2.7.10	Y–Y Transformers	193
8.2.7.11	Summary	194

8.2.8	Transmission of Voltage and Current across Two-Winding Transformers	197
8.2.8.1	Y- Δ and Δ -Y Transformers	197
8.2.8.2	Y-Y, Δ - Δ , Z-Z, Δ -Z and Z- Δ Transformers	204
8.2.8.3	The Transmission Matrices $\mathbf{T}$ and $\mathbf{T}_e$. . .	207
8.2.9	Transmission Matrices and the Phase Admittance Matrix	208
8.3	Modelling of Three-Winding Transformers	209
8.4	Modelling of Four-Winding Transformers	213
8.5	Summary	216
	Problems	216
9.	Modelling of Transmission Lines / Cables	221
9.1	Introduction	221
9.2	Skin Effect	221
9.3	Modelling of Power Lines	221
9.4	Line's Series Impedance	222
9.5	Mutual Coupling between Conductors	227
9.6	Mutually-Coupled Lines	228
9.7	Line's Shunt Capacitance	229
9.8	Surge Impedance and Velocity of Propagation	232
9.9	Line's Series Impedance and Shunt Capacitance – Single-Phase Equivalents	232
9.10	The Transmission (ABCD) Matrix	233
9.11	The Admittance Matrix	234
9.12	Conversion between the Transmission and Admittance Matrices	235
9.13	The Nominal π Model – Single-Phase Equivalent	241
9.14	The Equivalent π Model – Voltage and Current along the Line	241
9.15	Lossless Lines	251
9.16	The Equivalent π Model – Single-Phase Equivalent	251
9.17	Variations in the Network's Short-Circuit Capacity	260
9.18	Examples – The Nominal and Equivalent π Models	260
9.18.1	A 300 kV, 300 km Transmission Line	260
9.18.2	A 6.6 kV, 30 km Cable	266
9.19	Summary	268
	Problems	269
10.	Power System Harmonic Studies – A Simple Approach . . .	275
10.1	Introduction	275
10.2	Harmonic Analysis Using a Computer Program	275
10.3	Harmonic Analysis Using a Spreadsheet	275
10.3.1	Input Data	276

10.3.2	Network Analysis	276
10.3.3	Harmonic Filter Design	281
10.4	Harmonic Distortion Limits	283
10.5	Harmonic Filter Rating	283
10.6	Practical Considerations	290
10.7	A Sample Harmonic Study	291
10.8	Harmonic Study for a 300-22 kV Industrial Power System ..	296
10.8.1	Harmonic Analysis	300
10.8.1.1	System Impedances	300
10.8.1.2	Impedance Scan	302
10.8.1.3	Harmonic Injection	303
10.8.2	Effect of Varying Short-Circuit Capacity	305
10.8.3	Effect of Transformer Outage	307
10.8.4	Effect of Increased Transformer Impedance	308
10.8.5	Effect of Increased Motor Load	310
10.8.6	Effect of Increased Passive Load	312
10.8.7	Harmonic Filter Rating	314
10.9	Harmonic Study for a 300-33 kV Industrial Power System ..	315
10.9.1	System Description	315
10.9.2	Harmonic Analysis	321
10.9.2.1	System Impedances	321
10.9.2.2	Impedance Scan	323
10.9.2.3	Harmonic Injection	324
10.9.3	Output Results	324
10.9.4	Harmonic Filter Rating	326
10.9.5	Variations in the HV Network Short-Circuit Capacity ..	327
10.9.6	Effect of Transformer Outage	332
10.9.7	Effect of Reduced Transformer Impedance	334
10.9.8	Effect of Increased Motor Load	336
10.9.9	Effect of Increased Passive Load	336
10.10	Harmonic Study for a 132-22 kV Industrial Power System ..	339
10.10.1	Harmonic Analysis	344
10.10.1.1	System Impedances	344
10.10.1.2	Impedance Scan	346
10.10.1.3	Harmonic Injection	348
10.10.2	Effect of Varying Short-Circuit Capacity	349
10.10.3	Effect of Transformer Outage	352
10.10.4	Effect of Increased Transformer Impedance	354
10.10.5	Effect of Increased Motor Load	355
10.10.6	Effect of Increased Passive Load	356
10.11	Harmonic Study for a 400-33 kV Industrial Power System ..	358
10.11.1	Harmonic Analysis	361
10.11.1.1	System Impedances	361
10.11.1.2	Impedance Scan	363

10.11.1.3	Harmonic Injection	363
10.11.1.4	Output Results	364
10.12	Harmonic Study for a Low-Voltage System	366
10.12.1	Harmonic Analysis	368
10.12.1.1	System Impedances	368
10.12.1.2	Impedance Scan	370
10.12.1.3	Harmonic Injection	371
10.12.1.4	Output Results	371
10.13	Summary	373
	Problems	373
	Bibliography	376
	Appendices	381
A.	A Review of Transformation and Symmetrical Components	383
A.1	The Transformation Matrix A	385
A.2	Symmetrical Components	386
B.	Phase and Sequence Admittance Matrices for Three-Phase Transformers	391
B.1	$Y_g - \Delta$ Transformers	393
B.1.1	Y_{gd1} Transformers	394
B.1.2	Y_{gd3} Transformers	396
B.1.3	Y_{gd5} Transformers	398
B.1.4	Y_{gd7} Transformers	400
B.1.5	Y_{gd9} Transformers	402
B.1.6	Y_{gd11} Transformers	404
B.2	$Y - \Delta$ Transformers	406
B.2.1	Y_{d1} Transformers	406
B.2.2	Y_{d3} Transformers	408
B.2.3	Y_{d5} Transformers	410
B.2.4	Y_{d7} Transformers	412
B.2.5	Y_{d9} Transformers	414
B.2.6	Y_{d11} Transformers	416
B.3	$\Delta - Y_g$ Transformers	418
B.3.1	D_{yg1} Transformers	419
B.4	$\Delta - Y$ Transformers	421
B.4.1	D_{y1} Transformers	421
B.5	$Y_g - Y_g$ Transformers	423
B.5.1	Y_{gyg0} Transformers	424
B.5.2	Y_{gyg2} Transformers	426
B.5.3	Y_{gyg4} Transformers	428
B.5.4	Y_{gyg6} Transformers	430
B.5.5	Y_{gyg8} Transformers	432

	B.5.6	$Y_{gy}10$ Transformers	434
B.6		Y_g-Y Transformers	436
	B.6.1	$Y_{gy}0$ Transformers	436
	B.6.2	$Y_{gy}2$ Transformers	438
	B.6.3	$Y_{gy}4$ Transformers	440
	B.6.4	$Y_{gy}6$ Transformers	442
	B.6.5	$Y_{gy}8$ Transformers	444
	B.6.6	$Y_{gy}10$ Transformers	446
B.7		$Y-Y_g$ Transformers	448
	B.7.1	$Y_{yg}0$ Transformers	448
B.8		$Y-Y$ Transformers	450
	B.8.1	$Yy0$ Transformers	450
	B.8.2	$Yy2$ Transformers	452
	B.8.3	$Yy4$ Transformers	454
	B.8.4	$Yy6$ Transformers	456
	B.8.5	$Yy8$ Transformers	458
	B.8.6	$Yy10$ Transformers	460
B.9		$\Delta-\Delta$ Transformers	462
	B.9.1	$Dd0$ Transformers	463
	B.9.2	$Dd2$ Transformers	465
	B.9.3	$Dd4$ Transformers	467
	B.9.4	$Dd6$ Transformers	469
	B.9.5	$Dd8$ Transformers	471
	B.9.6	$Dd10$ Transformers	473
B.10		Summary	475
C.		Transmission Matrices for Three-Phase Transformers	479
C.1		$\Delta-Y$ and $Y-\Delta$ Transformers	481
	C.1.1	$Y-\Delta$ Transformers	482
		C.1.1.1 $Yd1$ Transformers	482
		C.1.1.2 $Yd3$ Transformers	483
		C.1.1.3 $Yd5$ Transformers	484
		C.1.1.4 $Yd7$ Transformers	485
		C.1.1.5 $Yd9$ Transformers	486
		C.1.1.6 $Yd11$ Transformers	487
	C.1.2	$\Delta-Y$ Transformers	488
		C.1.2.1 $Dy1$ Transformers	488
		C.1.2.2 $Dy3$ Transformers	489
		C.1.2.3 $Dy5$ Transformers	490
		C.1.2.4 $Dy7$ Transformers	491
		C.1.2.5 $Dy9$ Transformers	492
		C.1.2.6 $Dy11$ Transformers	493
	C.1.3	Summary	494
C.2		$Y-Y$, $\Delta-\Delta$, $Z-Z$, $\Delta-Z$ and $Z-\Delta$ Transformers	496
	C.2.1	$Yy0$ and $Dd0$ Transformers	498

C.2.2	Yy2 and Dd2 Transformers	499
C.2.3	Yy4 and Dd4 Transformers	500
C.2.4	Yy6 and Dd6 Dz6 Transformers	501
C.2.5	Yy8 and Dd8 Dz8 Transformers	502
C.2.6	Yy10 and Dd10 Transformers	503
C.2.7	Summary	504
C.3	The Transmission Matrices $\mathbf{T}$ and $\mathbf{T}_e$	506