ELECTRIC DRIVES

Ion Boldea
Fellow IEEE
University Politehnica
Timisoara, Romania

S. A. Nasar
Life Fellow IEEE
University of Kentucky
Lexington, KY

FH Vorarlberg
Bibliothek

CRC Press
Boca Raton London New York Washington, D.C.

CONTENTS

Preface

1. ENERGY CONVERSION IN ELECTRIC DRIVES 1
   - 1.1. Electric drives — a definition 1
   - 1.2. Application range of electric drives 2
   - 1.3. Energy savings pays off rapidly 4
   - 1.4. Global energy savings through PEC drives 5
   - 1.5. Motor / mechanical load match 7
     - 1.5.1. Typical load torque /speed curves 7
   - 1.6. Motion / time profile match 8
   - 1.7. Load dynamics and stability 11
   - 1.8. Multiquadrant operation 16
   - 1.9. Summary 17
   - 1.10. Problems 18

   Selected references 19

2. ELECTRIC MOTORS FOR DRIVES 21
   - 2.1. Electric drives — a typical configuration 21
   - 2.2. Electric motors for drives 22
   - 2.3. D.c. brush motors 23
   - 2.4. Conventional a.c. motors 24
   - 2.5. Power electronic converter dependent motors 26
   - 2.6. Summary 28

   Selected references 29

3. POWER ELECTRONIC CONVERTERS (PECs) FOR DRIVES 31
   - 3.1. Power electronic switches (PESs) 31
   - 3.2. The line frequency diode rectifier for constant d.c. output voltage V_d 34
   - 3.3. Line current harmonics with diode rectifiers 36
   - 3.4. Current commutation with I_d = ct. and L_s * 0 39
   - 3.5. Three phase diode rectifiers 40
   - 3.6. Phase controlled rectifiers (a.c.-d.c. converters) 43
   - 3.7. D.c. - d.c. converters (choppers) 45
   - 3.8. D.c. - a.c. converters (inverters) 46
   - 3.9. Direct a.c.-a.c. converters 49
   - 3.10. Summary 50
   - 3.11. Problems 51

   Selected references 52

4. D.C. BRUSH MOTOR DRIVES 53
   - 4.1. Basic topologies 53
   - 4.2. The motion induced voltage (e.m.f.) 55
   - 4.3. Performance equations - d-q model 56
   - 4.4. Steady state motor characteristics 57

4.5. D.c. brush motor losses 58
4.6. Varying the speed 61
4.7. Transient operation for constant flux 64
4.8. P.M. brush motor transients 66
4.9. Transient operation for variable flux 68
4.10. Speed / excitation transfer function 69
4.11. The d.c. brush series motor 70
4.12. Summary 72
4.13. Problems 72
Selected references 73
CONTROLLED RECTIFIER D.C. BRUSH MOTOR DRIVES 75
5.1. Introduction 75
5.2. Performance indices 76
5.3. Single PES controlled rectifier 78
5.4. The single-phase semiconverter 80
5.5. The single-phase full converter 83
5.6. The three-phase semiconverter 86
5.7. The three-phase full converter - motor side 88
5.8. The three-phase full converter - source-side aspects 91
5.9. The dual converter - four-quadrant operation 94
5.10. Summary 96
5.11. Problems 96
Selected references 98
CHOPPER-CONTROLLED D.C. BRUSH MOTOR DRIVES 99
6.1. Introduction 99
6.2. The first quadrant (step-down) chopper 103
6.3. The second quadrant (step-up) chopper for generator braking 105
6.4. The two-quadrant chopper 107
6.5. The four-quadrant chopper 110
6.6. The input filter 113
6.7. Digital simulation through Matlab-Simulink 116
6.8. Summary 118
6.9. Additional problems 119
Selected references 120
7. CLOSED LOOP MOTION CONTROL IN ELECTRIC DRIVES 121
7.1. Introduction 121
7.2. The cascaded motion control 121
7.2.1. The torque loop 122
7.2.2. The speed loop 124
7.2.3. Digital position control 125
7.2.4. Positioning precision 128
7.3. State-space motion control 129
7.4. Toraue Derturbation observers 131

7.5. Path tracking 133
7.6. Force control 134
7.7. Sliding-mode motion control 135
7.8. Motion control by fuzzy systems 142
7.9. Motion control through neural networks 148
7.10. Neuro-fuzzy networks 150
7.10.1. Applications of neural networks 151
7.11. Summary 151
7.12. Problems 151
Selected references 152
INDUCTION MOTORS FOR DRIVES 153
8.1. The stator and its traveling field 153
8.2. The cage and wound rotors are equivalent 155
8.3. Slot shaping depends on application and power level 156
8.4. The inductance matrix 157
8.5. Reducing the rotor to stator , 159
8.6. The phase coordinate model goes to 8^{th} order 160
8.7. The space-phasor model 161
8.8. The space-phasor diagram for electrical transients 166
8.9. Electrical transients with flux linkages as variables 167
8.10. Complex eigen-values for electrical transients 168
8.11. Electrical transients for constant rotor flux 169
8.12. Steady state: it is D.C. in synchronous coordinates 170
8.13. No-load ideal speed may go under or over conventional value co, 173
8.14. Motoring, generating, a.c. braking 177
8.15. D.c. braking: zero braking torque at zero speed 178
8.16. Speed control methods 180
8.17. V,/f| torque/speed curves 181
8.18. Only for constant rotor flux torque/speed curves are linear 182
8.19. Constant stator flux torque/speed curves have two breakdown points 183
8.20. Summary 184
8.21. Problems 185
Selected references 186
PWM INVERTER-FED INDUCTION MOTOR DRIVES 187
9.1. Introduction 187
9.2. Vector control - general flux orientation 188
9.3. General current decoupling 190
9.4. Parameter detuning effects in rotor flux orientation current decoupling 192
9.5. Direct versus indirect vector current decoupling 194
9.6. A.c. versus d.c. current controllers 195

9.7. Voltage decoupling 196
9.8. Voltage and current limitations for the torque and speed control range 199
9.9. Impressing voltage and currents through PWM 206
9.9.1. Switching state voltage vectors 206
9.9.2. Open-loop space-vector PWM 208
9.9.3. Closed-loop PWM 211
9.10. Indirect vector a.c. current control — a case study 213
9.11. Flux observers for direct vector control with motion sensors 217
9.11.1. Open-loop flux observers 218
9.11.2. Closed-loop flux observers 219
9.12. Indirect vector synchronous current control with speed sensor — a case study 220
9.13. Flux and speed observers in sensorless drives 224
9.13.1. Performance criteria 225
9.13.2. A classification of speed observers 225
9.13.3. Speed estimators 225
9.13.4. Model reference adaptive systems (MRAS) 226
9.13.5. Luenberger speed observers 227
9.13.6. Rotor slots ripple speed estimators 229
9.14. Direct torque and flux control (DTFC) 229
9.14.1. DTFC principle 231
9.15. Sensorless DTFC: a case study 233
9.16. Feedback linearized control 239
9.17. Scalar (V,/f,) control 239
9.18. Self commisioning 244
9.19. Summary 248
9.20. Problems 250
Selected references 250
10. SYNCHRONOUS'MOTORS FOR DRIVES 253
10.1. Introduction 253
10.2. Construction aspects 254
10.3. Pulsating torque 256
10.4. The phase coordinate model 257
10.5. The space phasor (d-q) model 259
10.6. Steady state operation 264
10.7. To vary speed variable frequency is mandatory 265
10.8. Summary 275
10.9. Problems 276
Selected references 277
11. PM AND RELUCTANCE SYNCHRONOUS MOTOR DRIVES 279
11.1. Introduction 279
11.2. PM-SM drives: classifications 279

11.3. Rectangular current control (brushless d.c. motor drives) 282
11.3.1. Ideal brushless d.c. motor waveforms 282
11.3.2. The rectangular current control system 285
11.3.3. The hysteresis current controller 286
11.3.4. Practical performance 289
11.3.5. Extending the torque/speed domain 290
11.4. Vector (sinusoidal) control 295
11.4.1. Optimum i_d - i_q relationships 296
11.4.2. The indirect vector current control 299
11.4.3. Indirect voltage and current vector control 300
11.4.4. Fast response PM- SM drives: surface PM rotor motors with predictive control 301
11.5. Direct torque and flux control (DTFC) of PM-SMs 309
11.5.1. The stator flux and torque observer 310
11.6. Sensorless control of PM-SMs 312
11.6.1. Initial rotor position detection 314
11.7. Reluctance synchronous motor (RSM) drives 315
11.7.1. RSM vector control principles 315
11.7.2. Indirect vector current control of RSM 318
11.7.3. Direct torque and flux control (DTFC) of RSM 321
11.7.4. Sensorless control of RSM 322
11.8. Summary 323
11.9. Problems 325
Selected references 325
12. SWITCHED RELUCTANCE MOTOR (SRM) DRIVES 327
12.1. Introduction 327
12.2. Construction and functional aspects 327
12.3. Average torque and energy conversion ratio 331
12.4. The peak kW / kVA ratio 333
12.5. The commutation windings 334
12.6. SRM modelling 335
12.7. The flux-current-position curve fitting 337
12.8. SRM drives 338
12.9. General purpose drive with position sensor 339
12.10. High grade (servo) drives 344
12.11. Sensorless SRM drives 347
12.12. The voltage-current model-based position - speed observer 349
12.13. Summary 350
12.14. Problems 351
Selected references 352
13. PRACTICAL ISSUES WITH PWM CONVERTER MOTOR DRIVES 353
13.1. Introduction 353

13.2. The basic PWM converter drive 353
13.3. Line current harmonics 354
13.4. Long motor power cables: voltage reflection and attenuation 359
13.5. Motor model for ultrahigh frequency 363
13.6. Common mode voltage: motor model and consequences 364
13.7. Common mode (leakage) stator current reduction 366
13.8. Bearing currents 368
13.9. Reducing the bearing currents 368
13.10. Electromagnetic interference 369
13.11. The audible noise 370
13.12. Losses in PWM converter drives 371
13.13. Summary 371
13.14. Problems 372
Selected references 373
14. LARGE POWER DRIVES 375
14.1. Power and speed limits: moving up 375
14.2. Voltage source converter synchronous motor drives 377
14.3. Vector control in voltage source converter SM drives 379
14.4. Direct torque and flux control (DTFC) 383
14.4.1. Sensorless control 385
14.5. Large motor drives: working less time per day is better 386
14.6. Rectifier-current source inverter SM drives — basic scheme 386
14.7. Rectifier-CSI-SM drive — steady state with load commutation 388
14.7.1. Commutation and steady state equations 389
14.7.2. Ideal no load speed 393
14.7.3. Speed control options 393
14.7.4. Steady-state speed/torque curves 394
14.7.5. Line commutation during starting 395
14.7.6. Drive control loops 396
14.7.7. Direct torque and flux control (DTFC) of rectifier-CSI-SM drives 397
14.8. Sub and hyper-synchronous IM cascade drives 399
14.8.1. Limited speed control range for lower PECs ratings 399
14.8.2. Sub- and hyper-operation modes 401
14.8.3. Sub- and hyper-IM cascade control 403
14.9. Summary 406
14.10. Problems 407
Selected references 408
Index 409