
ELECTRIC MOTOR DRIVES

Modeling, Analysis, and Control

R. Krishnan

Virginia Tech, Blacksburg, VA



Upper Saddle River, New Jersey 07458

Contents

Symbols	xxi
1 Introduction	1
1.1 Introduction	1
1.2 Power Devices and Switching	2
1.2.1 <i>Power Devices</i>	2
1.2.2 <i>Switching of Power Devices</i>	6
1.3 Motor Drive	7
1.3.1 <i>Electric Machines</i>	8
1.3.2 <i>Power Converters</i>	12
1.3.3 <i>Controllers</i>	13
1.3.4 <i>Load</i>	14
1.4 Scope of the Book	16
1.5 References	17
2 Modeling of DC Machines	18
2.1 Theory of Operation	18
2.2 Induced Emf	19
2.3 Equivalent Circuit and Electromagnetic Torque	21
2.4 Electromechanical Modeling	22
2.5 State-Space Modeling	22
2.6 Block Diagram and Transfer Functions	23
2.7 Field Excitation	24
2.7.1 <i>Separately-Excited DC Machine</i>	24
2.7.2 <i>Shunt-Excited DC Machine</i>	27
2.7.3 <i>Series-Excited DC Machine</i>	27

2.7.4	<i>DC Compound Machine</i>	30
2.7.5	<i>Permanent-Magnet DC Machine</i>	30
2.8	Measurement of Motor Constants	31
2.8.1	<i>Armature Resistance</i>	31
2.8.2	<i>Armature Inductance</i>	32
2.8.3	<i>Emf Constant</i>	32
2.9	Flow Chart for Computation	33
2.10	Suggested Readings	35
2.11	Discussion Questions	35
2.12	Exercise Problems	35
3	Phase-Controlled DC Motor Drives	36
3.1	Introduction	36
3.2	Principles of DC Motor Speed Control	37
3.2.1	<i>Fundamental Relationship</i>	37
3.2.2	<i>Field Control</i>	37
3.2.3	<i>Armature Control</i>	38
3.2.4	<i>Armature and Field Controls</i>	38
3.2.5	<i>Four-Quadrant Operation</i>	43
3.3	Phase-Controlled Converters	47
3.3.1	<i>Single-Phase-Controlled Converter</i>	47
3.3.2	<i>Three-Phase-Controlled Converter</i>	51
3.3.3	<i>Control Circuit</i>	54
3.3.4	<i>Control Modeling of the Three-Phase Converter</i>	55
3.3.5	<i>Current Source</i>	56
3.3.6	<i>Half-Controlled Converter</i>	57
3.3.7	<i>Converters with Freewheeling</i>	58
3.3.8	<i>Converter Configuration for a Four-Quadrant DC Motor Drive</i>	59
3.4	Steady-State Analysis of the Three-Phase Converter-Controlled DC Motor Drive	60
3.4.1	<i>Average Analysis</i>	60
3.4.2	<i>Steady-State Solution, Including Harmonics</i>	64
3.4.3	<i>Critical Triggering Angle</i>	67
3.4.4	<i>Discontinuous Current Conduction</i>	67
3.5	Two-Quadrant, Three-Phase Converter-Controlled DC Motor Drive	71
3.6	Transfer Functions of the Subsystems	73
3.6.1	<i>DC Motor and Load</i>	73
3.6.2	<i>Converter</i>	75
3.6.3	<i>Current and Speed Controllers</i>	75
3.6.4	<i>Current Feedback</i>	75
3.6.5	<i>Speed Feedback</i>	75
3.7	Design of Controllers	76
3.7.1	<i>Current Controller</i>	76
3.7.2	<i>First-Order Approximation of Inner Current Loop</i>	78
3.7.3	<i>Speed Controller</i>	79

3.8	Two-Quadrant DC Motor Drive with Field Weakening	88
3.9	Four-Quadrant DC Motor Drive	89
3.10	Converter Selection and Characteristics	91
3.11	Simulation of the One-Quadrant DC Motor Drive	92
3.11.1	<i>The Motor Equations</i>	92
3.11.2	<i>Filter in the Speed-Feedback Loop</i>	93
3.11.3	<i>Speed Controller</i>	93
3.11.4	<i>Current Reference Generator</i>	94
3.11.5	<i>Current Controller</i>	94
3.11.6	<i>Flowchart for Simulation</i>	95
3.11.7	<i>Simulation Results</i>	97
3.12	Harmonics and Associated Problems	98
3.12.1	<i>Harmonic Resonance</i>	98
3.12.2	<i>Twelve-Pulse Converter for DC Motor Drives</i>	102
3.12.3	<i>Selective Harmonic Elimination and Power-Factor Improvement by Switching</i>	104
3.13	Sixth-Harmonic Torque	107
3.13.1	<i>Continuous Current-Conduction Mode</i>	107
3.13.2	<i>Discontinuous Current-Conduction Mode</i>	110
3.14	Application Considerations	114
3.15	Applications	115
3.16	Parameter Sensitivity	118
3.17	Research Status	119
3.18	Suggested Readings	119
3.19	Discussion Questions	120
3.20	Exercise Problems	121

4 Chopper-Controlled DC Motor Drive

124

4.1	Introduction	124
4.2	Principle of Operation of the Chopper	124
4.3	Four-Quadrant Chopper Circuit	126
4.3.1	<i>First-Quadrant Operation</i>	126
4.3.2	<i>Second-Quadrant Operation</i>	129
4.3.3	<i>Third-Quadrant Operation</i>	130
4.3.4	<i>Fourth-Quadrant Operation</i>	131
4.4	Chopper for Inversion	132
4.5	Chopper With Other Power Devices	133
4.6	Model of the Chopper	133
4.7	Input to the Chopper	133
4.8	Other Chopper Circuits	135
4.9	Steady-State Analysis of Chopper-Controlled DC Motor Drive	136
4.9.1	<i>Analysis by Averaging</i>	136
4.9.2	<i>Instantaneous Steady-State Computation</i>	137

4.9.3	<i>Continuous Current Conduction</i>	137
4.9.4	<i>Discontinuous Current Conduction</i>	140
4.10	Rating of the Devices	143
4.11	Pulsating Torques	144
4.12	Closed-Loop Operation	151
4.12.1	<i>Speed-Controlled Drive System</i>	151
4.12.2	<i>Current Control Loop</i>	151
4.12.3	<i>Pulse-Width-Modulated Current Controller</i>	152
4.12.4	<i>Hysteresis Current Controller</i>	155
4.12.5	<i>Modeling of Current Controllers</i>	156
4.12.6	<i>Design of Current Controller</i>	157
4.12.7	<i>Design of Speed Controller by Symmetric Optimum Method</i>	158
4.13	Dynamic Simulation of the Speed-Controlled DC Motor Drive	160
4.13.1	<i>Motor Equations</i>	161
4.13.2	<i>Speed Feedback</i>	161
4.13.3	<i>Speed Controller</i>	162
4.13.4	<i>Command Current Generator</i>	162
4.13.5	<i>Current Controller</i>	163
4.13.6	<i>System Simulation</i>	163
4.14	Application	167
4.15	Suggested Readings	170
4.16	Discussion Questions	171
4.17	Exercise Problems	172

5 Polyphase Induction Machines

174

5.1	Introduction	174
5.2	Construction and Principle of Operation	175
5.2.1	<i>Machine Construction</i>	175
5.2.2	<i>Principle of Operation</i>	180
5.3	Induction Motor Equivalent Circuit	181
5.4	Steady-State Performance Equations of the Induction Motor	184
5.5	Steady-State Performance	188
5.6	Measurement of Motor Parameters	193
5.6.1	<i>Stator Resistance</i>	193
5.6.2	<i>No-Load Test</i>	193
5.6.3	<i>Locked-Rotor Test</i>	194
5.7	Dynamic Modeling of Induction Machines	196
5.7.1	<i>Real-Time Model of a Two-Phase Induction Machine</i>	197
5.7.2	<i>Transformation to Obtain Constant Matrices</i>	200
5.7.3	<i>Three-Phase to Two-Phase Transformation</i>	203
5.7.4	<i>Power Equivalence</i>	209
5.7.5	<i>Generalized Model in Arbitrary Reference Frames</i>	209
5.7.6	<i>Electromagnetic Torque</i>	212
5.7.7	<i>Derivation of Commonly Used Induction Motor Models</i>	213

5.7.7.1	Stator Reference Frames Model	213
5.7.7.2	Rotor Reference Frames Model	214
5.7.7.3	Synchronously Rotating Reference Frames Model	215
5.7.8	<i>Equations in Flux Linkages</i>	218
5.7.9	<i>Per-Unit Model</i>	220
5.8	Dynamic Simulation	223
5.9	Small-Signal Equations of the Induction Machine	226
5.9.1	<i>Derivation</i>	226
5.9.2	<i>Normalized Small-Signal Equations</i>	234
5.10	Evaluation of Control Characteristics of the Induction Machine	236
5.10.1	<i>Transfer Functions and Frequency Responses</i>	236
5.10.2	<i>Computation of Time Responses</i>	238
5.11	Space-Phasor Model	242
5.11.1	<i>Principle</i>	242
5.11.2	<i>DQ Flux-Linkages Model Derivation</i>	243
5.11.3	<i>Root Loci of the DQ Axes-Based Induction Machine Model</i>	244
5.11.4	<i>Space-Phasor Model Derivation</i>	246
5.11.5	<i>Root Loci of the Space-Phasor Induction Machine Model</i>	248
5.11.6	<i>Expression for Electromagnetic Torque</i>	249
5.11.7	<i>Analytical Solution of Machine Dynamics</i>	252
5.11.8	<i>Signal-Flow Graph of the Space-Phasor-Modeled Induction Motor</i>	253
5.12	Control Principle of the Induction Motor	254
5.13	References	257
5.14	Discussion Questions	258
5.15	Exercise Problems	259
6	Phase-Controlled Induction Motor Drives	262
6.1	Introduction	262
6.2	Stator-Voltage Control	263
6.2.1	<i>Power Circuit and Gating</i>	263
6.2.2	<i>Reversible Controller</i>	263
6.2.3	<i>Steady-State Analysis</i>	265
6.2.4	<i>Approximate Analysis</i>	267
6.2.4.1	Motor Model and Conduction Angle	267
6.2.4.2	Fourier Resolution of Voltage	269
6.2.4.3	Normalized Currents	271
6.2.4.4	Steady-State Performance Computation	272
6.2.4.5	Limitations	273
6.2.5	<i>Torque-Speed Characteristics with Phase Control</i>	273
6.2.6	<i>Interaction of the Load</i>	273
6.2.6.1	Steady-State Computation of the Load Interaction	275
6.2.7	<i>Closed-Loop Operation</i>	279
6.2.8	<i>Efficiency</i>	279
6.2.9	<i>Applications</i>	282
6.3	Slip-Energy Recovery Scheme	283
6.3.1	<i>Principle of Operation</i>	283

6.3.2	<i>Slip-Energy Recovery Scheme</i>	283
6.3.3	<i>Steady-State Analysis</i>	285
6.3.3.1	Range of Slip	287
6.3.3.2	Equivalent Circuit	287
6.3.3.3	Performance Characteristics	289
6.3.4	<i>Starting</i>	296
6.3.5	<i>Rating of the Converters</i>	296
6.3.5.1	Bridge-Rectifier Ratings	297
6.3.5.2	Phase-Controlled Converter	297
6.3.5.3	Filter Choke	297
6.3.6	<i>Closed-Loop Control</i>	298
6.3.7	<i>Sixth-Harmonic Pulsating Torques</i>	299
6.3.8	<i>Harmonic Torques</i>	303
6.3.9	<i>Static Scherbius Drive</i>	304
6.3.10	<i>Applications</i>	305
6.4	References	308
6.5	Discussion Questions	309
6.6	Exercise Problems	311

7 Frequency-Controlled Induction Motor Drives

313

7.1	Introduction	313
7.2	Static Frequency Changers	313
7.3	Voltage-Source Inverter	317
7.3.1	<i>Modified McMurray Inverter</i>	317
7.3.2	<i>Full-Bridge Inverter Operation</i>	319
7.4	Voltage-Source Inverter-Driven Induction Motor	320
7.4.1	<i>Voltage Waveforms</i>	320
7.4.2	<i>Real Power</i>	323
7.4.3	<i>Reactive Power</i>	323
7.4.4	<i>Speed Control</i>	324
7.4.5	<i>Constant Volts/Hz Control</i>	325
7.4.5.1	Relationship Between Voltage and Frequency	325
7.4.5.2	Implementation of Volts/Hz Strategy	328
7.4.5.3	Steady-State Performance	330
7.4.5.4	Dynamic Simulation	330
7.4.5.5	Small-Signal Responses	338
7.4.5.6	Direct Steady-State Evaluation	340
7.4.6	<i>Constant Slip-Speed Control</i>	346
7.4.6.1	Drive Strategy	346
7.4.6.2	Steady-State Analysis	347
7.4.7	<i>Constant-Air Gap-Flux Control</i>	350
7.4.7.1	Principle of Operation	350
7.4.7.2	Drive Strategy	350
7.4.8	<i>Torque Pulsations</i>	354
7.4.8.1	General	354
7.4.8.2	Calculation of Torque Pulsations	354
7.4.8.3	Effects of Time Harmonics	360

7.4.9	<i>Control of Harmonics</i>	362
7.4.9.1	General	362
7.4.9.2	Phase-Shifting Control	362
7.4.9.3	Pulse-Width Modulation (PWM)	365
7.4.10	<i>Steady-State Evaluation with PWM Voltages</i>	369
7.4.10.1	PWM Voltage Generation	369
7.4.10.2	Machine Model	370
7.4.10.3	Direct Evaluation of Steady-State Current Vector by Boundary-Matching Technique	372
7.4.10.4	Computation of Steady-State Performance	373
7.4.11	<i>Flux-Weakening Operation</i>	377
7.4.11.1	Flux Weakening	377
7.4.11.2	Calculation of Slip	379
7.4.11.3	Maximum Stator Frequency	380
7.5	Current-Source Induction Motor Drives	381
7.5.1	General	381
7.5.2	ASCI	382
7.5.2.1	Commutation	382
7.5.2.2	Phase-Sequence Reversal	383
7.5.2.3	Regeneration	384
7.5.2.4	Comparison of Converters for AC and DC Motor Drives	385
7.5.3	<i>Steady-State Performance</i>	385
7.5.4	<i>Direct Steady-State Evaluation of Six-Step Current-Source Inverter-Fed Induction Motor (CSIM) Drive System</i>	389
7.5.5	<i>Closed-Loop CSIM Drive System</i>	396
7.5.6	<i>Dynamic Simulation of the Closed-Loop CSIM Drive System</i>	398
7.6	Applications	405
7.7	References	406
7.8	Discussion Questions	407
7.9	Exercise Problems	409

8 Vector-Controlled Induction Motor Drives 411

8.1	Introduction	411
8.2	Principle of Vector Control	412
8.3	Direct Vector Control	415
8.3.1	<i>Description</i>	415
8.3.2	<i>Flux and Torque Processor</i>	416
8.3.2.1	Case (i): Terminal voltages	417
8.3.2.2	Case (ii): Induced emf from flux sensing coils or Hall sensors	420
8.3.3	<i>Implementation with Six-Step Current Source</i>	422
8.3.4	<i>Implementation with Voltage Source</i>	425
8.3.5	<i>Direct Vector (Self) Control in Stator Reference Frames with Space-Vector Modulation</i>	426
8.4	Derivation of Indirect Vector-Control Scheme	446
8.5	Indirect Vector-Control Scheme	448
8.6	An Implementation of an Indirect Vector-Control Scheme	450

8.7	Tuning of the Vector Controller	454
8.8	Flowchart for Dynamic Computation	457
8.9	Dynamic Simulation Results	458
8.10	Parameter Sensitivity of the Indirect Vector-Controlled Induction Motor Drive	461
8.10.1	<i>Parameter Sensitivity Effects When the Outer Speed Loop Is Open</i>	461
8.10.1.1	Expression for Electromagnetic Torque	461
8.10.1.2	Expression for the Rotor Flux Linkages	463
8.10.1.3	Steady-State Results	463
8.10.1.4	Transient Characteristics	466
8.10.2	<i>Parameter Sensitivity Effects on a Speed-Controlled Induction Motor Drive</i>	468
8.10.2.1	Steady-State Characteristics	469
8.10.2.2	Discussion on Transient Characteristics	473
8.10.2.3	Parameter Sensitivity of Other Motor Drives	474
8.11	Parameter Sensitivity Compensation	475
8.11.1	<i>Modified Reactive-Power Compensation Scheme</i>	476
8.11.2	<i>Parameter Compensation with Air Gap-Power Feedback Control</i>	477
8.11.2.1	Steady-State Performance	478
8.11.2.2	Dynamic Performance	482
8.12	Flux-Weakening Operation	484
8.12.1	<i>Flux-Weakening in Stator-Flux-Linkages-Controlled Schemes</i>	485
8.12.2	<i>Flux-Weakening in Rotor-Flux-Linkages-Controlled Scheme</i>	486
8.12.3	<i>Algorithm to Generate the Rotor Flux-Linkages Reference</i>	487
8.12.4	<i>Constant-Power Operation</i>	490
8.13	Speed-Controller Design for an Indirect Vector-Controlled Induction Motor Drive	492
8.13.1	<i>Block-Diagram Derivation</i>	492
8.13.1.1	Vector-Controlled Induction Machine	492
8.13.1.2	Inverter	495
8.13.1.3	Speed Controller	495
8.13.1.4	Feedback Transfer Functions	495
8.13.2	<i>Block-Diagram Reduction</i>	496
8.13.3	<i>Simplified Current-Loop Transfer Function</i>	496
8.13.4	<i>Speed-Controller Design</i>	499
8.14	Performance and Applications	502
8.14.1	<i>Application: Centrifuge Drive</i>	503
8.15	Research Status	504
8.16	References	505
8.17	Discussion Questions	509
8.18	Exercise Problems	511
9	Permanent-Magnet Synchronous and Brushless DC Motor Drives	
9.1	Introduction	513
9.2	Permanent Magnets and Characteristics	514

9.2.1	<i>Permanent Magnets</i>	514
9.2.2	<i>Air Gap Line</i>	514
9.2.3	<i>Energy Density</i>	517
9.2.4	<i>Magnet Volume</i>	518
9.3	Synchronous Machines with PMs	518
9.3.1	<i>Machine Configurations</i>	519
9.3.2	<i>Flux-Density Distribution</i>	521
9.3.3	<i>Line-Start PM Synchronous Machines</i>	522
9.3.4	<i>Types of PM Synchronous Machines</i>	523
9.4	Vector Control of PM Synchronous Motor (PMSM)	525
9.4.1	<i>Model of the PMSM</i>	525
9.4.2	<i>Vector Control</i>	527
9.4.3	<i>Drive-System Schematic</i>	529
9.5	Control Strategies	531
9.5.1	<i>Constant ($\delta = 90^\circ$) Torque-Angle Control</i>	531
9.5.2	<i>Unity-Power-Factor Control</i>	534
9.5.3	<i>Constant-Mutual-Flux-Linkages Control</i>	536
9.5.4	<i>Optimum-Torque-Per-Ampere Control</i>	537
9.6	Flux-Weakening Operation	539
9.6.1	<i>Maximum Speed</i>	539
9.6.2	<i>Direct Flux-Weakening Algorithm</i>	540
9.6.2.1	Control Scheme	542
9.6.2.2	Constant-Torque-Mode Controller	543
9.6.2.3	Flux-Weakening Controller	544
9.6.2.4	System Performance	545
9.6.3	<i>Indirect Flux-Weakening</i>	548
9.6.3.1	Maximum Permissible Torque	548
9.6.3.2	Speed-Control Scheme	549
9.6.3.3	Implementation Strategy	550
9.6.3.4	System Performance	552
9.6.3.5	Parameter Sensitivity	552
9.7	Speed-Controller Design	555
9.7.1	<i>Block-Diagram Derivation</i>	555
9.7.2	<i>Current Loop</i>	556
9.7.3	<i>Speed-Controller</i>	558
9.8	Sensorless Control	562
9.9	Parameter Sensitivity	567
9.9.1	<i>Ratio of Torque to Its Reference</i>	568
9.9.2	<i>Ratio of Mutual Flux-Linkages to Its Reference</i>	569
9.9.3	<i>Parameter Compensation Through Air Gap-Power Feedback Control</i>	569
9.9.3.1	Algorithm	571
9.9.3.2	Performance	572
9.10	PM Brushless DC Motor (PMBDCM)	577
9.10.1	<i>Modeling of PM Brushless DC Motor</i>	578
9.10.2	<i>The PMBDCM Drive Scheme</i>	580
9.10.3	<i>Dynamic Simulation</i>	581
9.10.4	<i>Commutation-Torque Ripple</i>	582

xx Contents

- 9.10.5 *Phase-Advancing* 586
- 9.10.6 *Normalized System Equations* 587
- 9.10.7 *Half-Wave PMBDCM Drives* 588
 - 9.10.7.1 Split-Supply Converter Topology 589
 - 9.10.7.2 C-Dump Topology 601
 - 9.10.7.3 Variable-DC-Link Converter Topology 607
- 9.10.8 *Sensorless Control of PMBDCM Drive* 611
- 9.10.9 *Torque-Smoothing* 614
- 9.10.10 *Design of Current and Speed Controllers* 614
- 9.10.11 *Parameter Sensitivity of the PMBDCM Drive* 614
- 9.11 References 615
- 9.12 Discussion Questions 616
- 9.13 Exercise Problems 620
- Index 621