Pulse Width Modulation For Power Converters

Principles and Practice

D. Grahame Holmes
Monash University
Melbourne, Australia

Thomas A. Lipo
University of Wisconsin
Madison, Wisconsin

IEEE Series on Power Engineering,
Mohamed E. El-Hawary, *Series Editor*

IEEE PRESS

A JOHN WILEY & SONS, INC., PUBLICATION

Contents

Preface xiii

Acknowledgments xiv

Nomenclature xv

Chapter 1 Introduction to Power Electronic Converters 1

1.1 Basic Converter Topologies 2
- 1.1.1 Switch Constraints 2
- 1.1.2 Bidirectional Chopper 4
- 1.1.3 Single-Phase Full-Bridge (H–Bridge) Inverter 5

1.2 Voltage Source/Stiff Inverters 7
- 1.2.1 Two-Phase Inverter Structure 7
- 1.2.2 Three-Phase Inverter Structure 8
- 1.2.3 Voltage and Current Waveforms in Square-Wave Mode 9

1.3 Switching Function Representation of Three-Phase Converters 14

1.4 Output Voltage Control 17
- 1.4.1 Volts/Hertz Criterion 17
- 1.4.2 Phase Shift Modulation for Single-Phase Inverter 17
- 1.4.3 Voltage Control with a Double Bridge 19

1.5 Current Source/Stiff Inverters 21

1.6 Concept of a Space Vector 24
- 1.6.1 d–q–0 Components for Three-Phase Sine Wave Source/Load 27
- 1.6.2 d–q–0 Components for Voltage Source Inverter Operated in Square-Wave Mode 30
- 1.6.3 Synchronously Rotating Reference Frame 35

1.7 Three-Level Inverters 38

1.8 Multilevel Inverter Topologies 42
- 1.8.1 Diode-Clamped Multilevel Inverter 42
- 1.8.2 Capacitor-Clamped Multilevel Inverter 49
- 1.8.3 Cascaded Voltage Source Multilevel Inverter 51

1.8.4 Hybrid Voltage Source Inverter 54
1.9 Summary 55

Chapter 2 Harmonic Distortion 57
2.1 Harmonic Voltage Distortion Factor 57
2.2 Harmonic Current Distortion Factor 61
2.3 Harmonic Distortion Factors for Three-Phase Inverters 64
2.4 Choice of Performance Indicator 67
2.5 WTHD of Three-Level Inverter 70
2.6 The Induction Motor Load 73
2.6.1 Rectangular Squirrel Cage Bars 73
2.6.2 Nonrectangular Rotor Bars 78
2.6.3 Per-Phase Equivalent Circuit 79
2.7 Harmonic Distortion Weighting Factors for Induction Motor Load 82
2.7.1 WTHD for Frequency-Dependent Rotor Resistance 82
2.7.2 WTHD Also Including Effect of Frequency-Dependent Rotor Leakage Inductance 84
2.7.3 WTHD for Stator Copper Losses 88
2.8 Example Calculation of Harmonic Losses 90
2.9 WTHD Normalization for PWM Inverter Supply 91
2.10 Summary 93

Chapter 3 Modulation of One Inverter Phase Leg 95
3.1 Fundamental Concepts of PWM 96
3.2 Evaluation of PWM Schemes 97
3.3 Double Fourier Integral Analysis of a Two-Level Pulse Width–Modulated Waveform 99
3.4 Naturally Sampled Pulse Width Modulation 105
3.4.1 Sine–Sawtooth Modulation 105
3.4.2 Sine–Triangle Modulation 114
3.5 PWM Analysis by Duty Cycle Variation 120
3.5.1 Sine–Sawtooth Modulation 120
3.5.2 Sine–Triangle Modulation 123

3.6 Regular Sampled Pulse Width Modulation....125
3.6.1 Sawtooth Carrier Regular Sampled PWM....130
3.6.2 Symmetrical Regular Sampled PWM....134
3.6.3 Asymmetrical Regular Sampled PWM....139
3.7 "Direct" Modulation....146
3.8 Integer versus Non-Integer Frequency Ratios....148
3.9 Review of PWM Variations....150
3.10 Summary....152

Chapter 4 Modulation of Single-Phase Voltage Source Inverters....155
4.1 Topology of a Single-Phase Inverter....156
4.2 Three-Level Modulation of a Single-Phase Inverter....157
4.3 Analytic Calculation of Harmonic Losses....169
4.4 Sideband Modulation....177
4.5 Switched Pulse Position....183
4.5.1 Continuous Modulation....184
4.5.2 Discontinuous Modulation....186
4.6 Switched Pulse Sequence....200
4.6.1 Discontinuous PWM — Single-Phase Leg Switched....200
4.6.2 Two-Level Single-Phase PWM....207
4.7 Summary....211

Chapter 5 Modulation of Three-Phase Voltage Source Inverters....215
5.1 Topology of a Three-Phase Inverter (VSI)....215
5.2 Three-Phase Modulation with Sinusoidal References....216
5.3 Third-Harmonic Reference Injection....226
5.3.1 Optimum Injection Level....226
5.3.2 Analytical Solution for Third-Harmonic Injection....230
5.4 Analytic Calculation of Harmonic Losses....241
5.5 Discontinuous Modulation Strategies....250
5.6 Triplen Carrier Ratios and Subharmonics....251
5.6.1 Triplen Carrier Ratios....251
5.6.2 Subharmonics....253

5.7 Summary 257

Chapter 6 Zero Space Vector Placement Modulation Strategies 259

6.1 Space Vector Modulation 259
6.1.1 Principles of Space Vector Modulation 259
6.1.2 SVM Compared to Regular Sampled PWM 265
6.2 Phase Leg References for Space Vector Modulation 267
6.3 Naturally Sampled SVM 270
6.4 Analytical Solution for SVM 272
6.5 Harmonic Losses for SVM 291
6.6 Placement of the Zero Space Vector 294
6.7 Discontinuous Modulation 299
6.7.1 120^{o} Discontinuous Modulation 299
6.7.2 60^{o} and 30^{o} Discontinuous Modulation 302
6.8 Phase Leg References for Discontinuous PWM 307
6.9 Analytical Solutions for Discontinuous PWM 311
6.10 Comparison of Harmonic Performance 322
6.11 Harmonic Losses for Discontinuous PWM 326
6.12 Single-Edge SVM 330
6.13 Switched Pulse Sequence 331
6.14 Summary 333

Chapter 7 Modulation of Current Source Inverters 337

7.1 Three-Phase Modulators as State Machines 338
7.2 Naturally Sampled CSI Space Vector Modulator 343
7.3 Experimental Confirmation 343
7.4 Summary 345

Chapter 8 Overmodulation of an Inverter 349

8.1 The Overmodulation Region 350
8.2 Naturally Sampled Overmodulation of One Phase Leg of an Inverter 351

8.3 Regular Sampled Overmodulation of One Phase Leg of an Inverter 356
8.4 Naturally Sampled Overmodulation of Single- and Three-Phase Inverters 360
8.5 PWM Controller Gain during Overmodulation 364
8.5.1 Gain with Sinusoidal Reference 364
8.5.2 Gain with Space Vector Reference 367
8.5.3 Gain with 60^{o} Discontinuous Reference 371
8.5.4 Compensated Modulation 373
8.6 Space Vector Approach to Overmodulation 376
8.7 Summary 382

Chapter 9 Programmed Modulation Strategies 383
9.1 Optimized Space Vector Modulation 384
9.2 Harmonic Elimination PWM 396
9.3 Performance Index for Optimality 411
9.4 Optimum PWM 416
9.5 Minimum-Loss PWM 421
9.6 Summary 430

Chapter 10 Programmed Modulation of Multilevel Converters 433
10.1 Multilevel Converter Alternatives 433
10.2 Block Switching Approaches to Voltage Control 436
10.3 Harmonic Elimination Applied to Multilevel Inverters 440
10.3.1 Switching Angles for Harmonic Elimination Assuming Equal Voltage Levels 440
10.3.2 Equalization of Voltage and Current Stresses 441
10.3.3 Switching Angles for Harmonic Elimination Assuming Unequal Voltage Levels 443
10.4 Minimum Harmonic Distortion 447
10.5 Summary 449

Chapter 11 Carrier-Based PWM of Multilevel Inverters 453
11.1 PWM of Cascaded Single-Phase H-Bridges 453

11.2 Overmodulation of Cascaded H-Bridges 465
11.3 PWM Alternatives for Diode-Clamped Multilevel Inverters ...467
11.4 Three-Level Naturally Sampled PD PWM 469
11.4.1 Contour Plot for Three-Level PD PWM 469
11.4.2 Double Fourier Series Harmonic Coefficients 473
11.4.3 Evaluation of the Harmonic Coefficients 475
11.4.4 Spectral Performance of Three-Level PD PWM 479
11.5 Three-Level Naturally Sampled APOD or POD PWM 481
11.6 Overmodulation of Three-Level Inverters 484
11.7 Five-Level PWM for Diode-Clamped Inverters 489
11.7.1 Five-level Naturally Sampled PD PWM 489
11.7.2 Five-Level Naturally Sampled APOD PWM 492
11.7.3 Five-Level POD PWM 497
11.8 PWM of Higher Level Inverters 499
11.9 Equivalent PD PWM for Cascaded Inverters 504
11.10 Hybrid Multilevel Inverter 507
11.11 Equivalent PD PWM for a Hybrid Inverter 517
11.12 Third-Harmonic Injection for Multilevel Inverters 519
11.13 Operation of a Multilevel Inverter with a Variable Modulation Index 526
11.14 Summary 528

Chapter 12 Space Vector PWM for Multilevel Converters 531
12.1 Optimized Space Vector Sequences 531
12.2 Modulator for Selecting Switching States 534
12.3 Decomposition Method 535
12.4 Hexagonal Coordinate System 538
12.5 Optimal Space Vector Position within a Switching Period 543
12.6 Comparison of Space Vector PWM to Carrier-Based PWM 545
12.7 Discontinuous Modulation in Multilevel Inverters 548
12.8 Summary 550

Chapter 13 Implementation of a Modulation Controller 555

13.1 Overview of a Power Electronic Conversion System 556

13.2 Elements of a PWM Converter System 557

13.2.1 VSI Power Conversion Stage 563

13.2.2 Gate Driver Interface 565

13.2.3 Controller Power Supply 567

13.2.4 I/O Conditioning Circuitry 568

13.2.5 PWM Controller 569

13.3 Hardware Implementation of the PWM Process 572

13.3.1 Analog versus Digital Implementation 572

13.3.2 Digital Timer Logic Structures 574

13.4 PWM Software Implementation 579

13.4.1 Background Software 580

13.4.2 Calculation of the PWM Timing Intervals 581

13.5 Summary 584

Chapter 14 Continuing Developments in Modulation 585

14.1 Random Pulse Width Modulation 586

14.2 PWM Rectifier with Voltage Unbalance 590

14.3 Common Mode Elimination 598

14.4 Four Phase Leg Inverter Modulation 603

14.5 Effect of Minimum Pulse Width 607

14.6 PWM Dead-Time Compensation 612

14.7 Summary 619

Appendix 1 Fourier Series Representation of a Double Variable Controlled Waveform 623

Appendix 2 Jacobi–Anger and Bessel Function Relationships 629

A2.1 Jacobi–Anger Expansions 629

A2.2 Bessel Function Integral Relationships 631

Appendix 3 Three-Phase and Half-Cycle Symmetry Relationships 635

Appendix 4 Overmodulation of a Single-Phase Leg.....637

A4.1 Naturally Sampled Double-Edge PWM 637

A4.1.1 Evaluation of Double Fourier Integral for Overmodulated Naturally Sampled PWM.....638

A4.1.2 Harmonic Solution for Overmodulated Single-Phase Leg under Naturally Sampled PWM.....646

A4.1.3 Linear Modulation Solution Obtained from Overmodulation Solution.....647

A4.1.4 Square-Wave Solution Obtained from Overmodulation Solution.....647

A4.2 Symmetric Regular Sampled Double-Edge PWM 649

A4.2.1 Evaluation of Double Fourier Integral for Overmodulated Symmetric Regular Sampled PWM.....650

A4.2.2 Harmonic Solution for Overmodulated Single-Phase Leg under Symmetric Regular Sampled PWM.....652

A4.2.3 Linear Modulation Solution Obtained from Overmodulation Solution.....653

A4.3 Asymmetric Regular Sampled Double-Edge PWM 654

A4.3.1 Evaluation of Double Fourier Integral for Overmodulated Asymmetric Regular Sampled PWM 655

A4.3.2 Harmonic Solution for Overmodulated Single-Phase Leg under Asymmetric Regular Sampled PWM 660

A4.3.3 Linear Modulation Solution Obtained from Overmodulation Solution.....661

Appendix 5 Numeric Integration of a Double Fourier Series Representation of a Switched Waveform.....663

A5.1 Formulation of the Double Fourier Integral 663

A5.2 Analytical Solution of the Inner Integral 666

A5.3 Numeric Integration of the Outer Integral 668

Bibliography.....671

Index.....715